

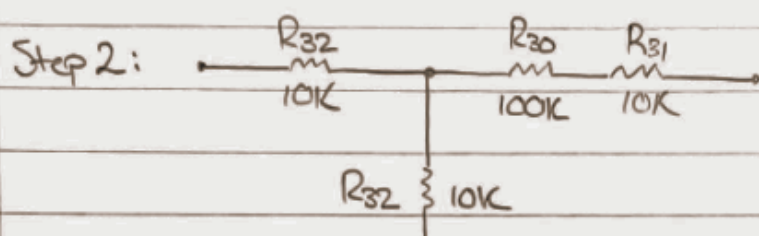
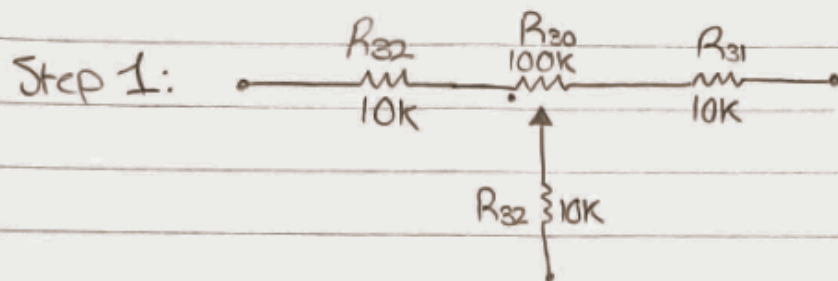


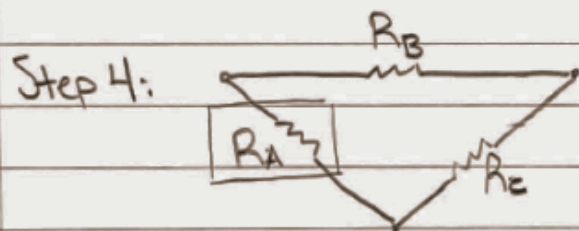Ben Damci : Z left Delta Transformation (B Band, 0 on left)



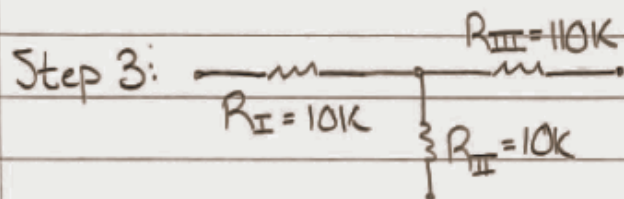Note: Due to my potentiometer orientation, 100% of the potentiometer's resistance is on the right branch.




Note: For this problem, we are interested in Z_{left} which is derived from R_A .

Step 5:

$$Z_{left} = (R_I + R_{II}) \left[1 + \frac{R_I \parallel R_{II}}{R_{III}} \right]$$
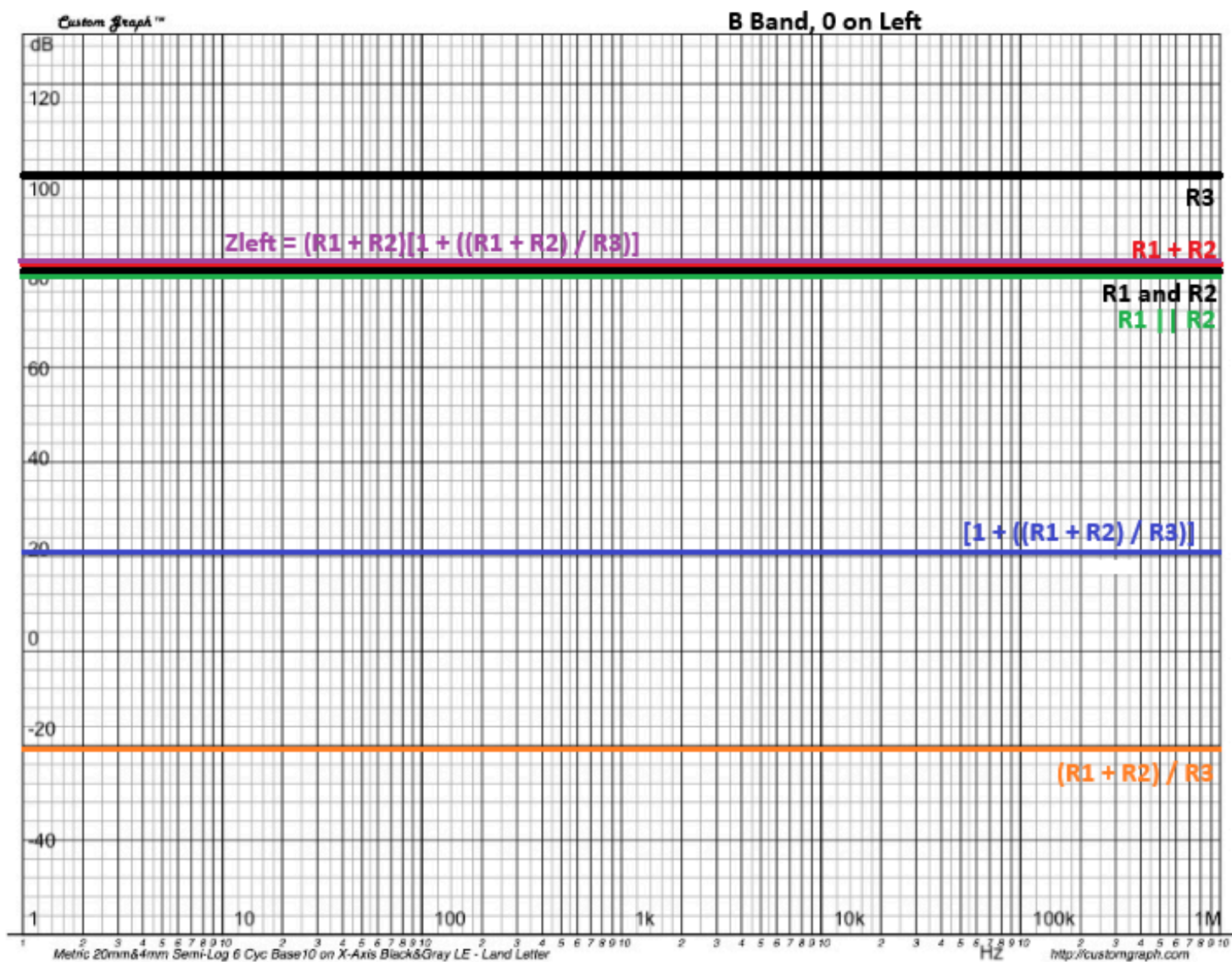
$$\begin{aligned} Z_{left} &= (10K + 10K) \left[1 + \frac{10K \parallel 10K}{110K} \right] \\ &= (20K) \left(1 + \left(\frac{10K \times 10K}{10K + 10K} \right) / 110K \right) \\ &= (20K) \left(1 + \frac{5K}{110K} \right) \approx \boxed{21K} \end{aligned}$$



R1 and R2 = 10K ohms -> $20\log_{10}(10000) = 80\text{dB}$

R3 = 110K ohms -> $20\log_{10}(110000) = 100.83 = 101\text{dB}$